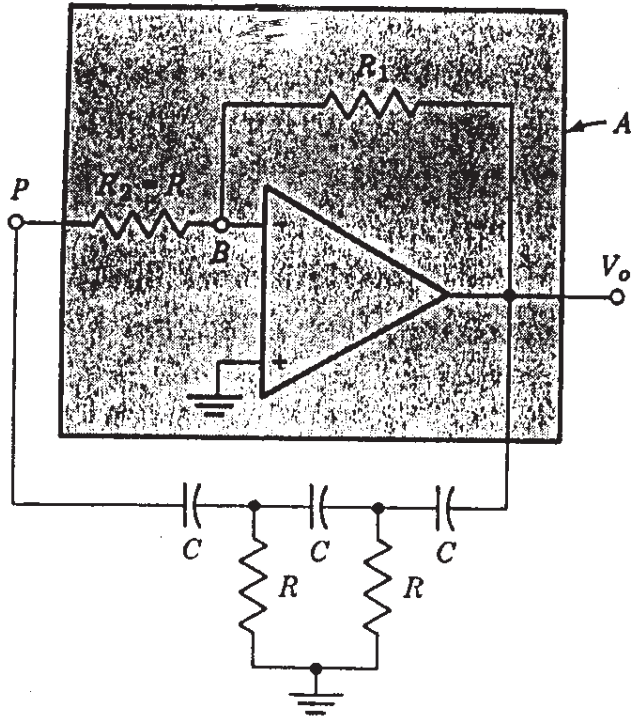


## Phase shift oscillator

**Example.** Let us consider the following phase shift oscillator:




The gain of the amplifier is:

$$A = -\beta$$


where

$$\beta = \frac{R_1}{R}$$

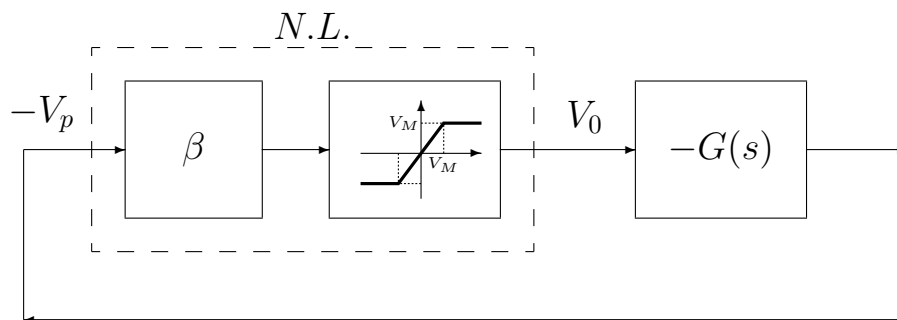- The feedback system can be described by the following block scheme:



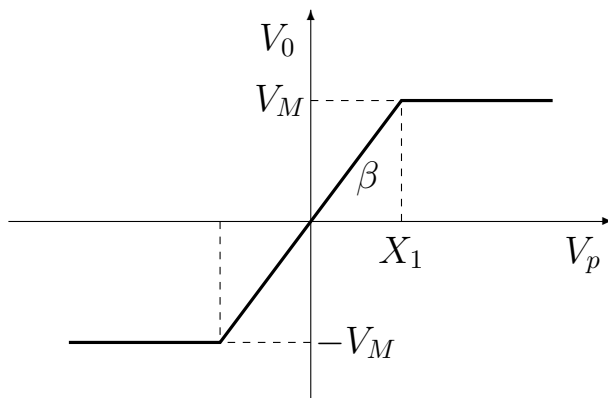
- The nonlinear element (N.L.) is a saturation with a central slope  $\beta$ :



$$X_1 = \frac{R V_M}{R_1}$$

$$\beta = \frac{R_1}{R}$$

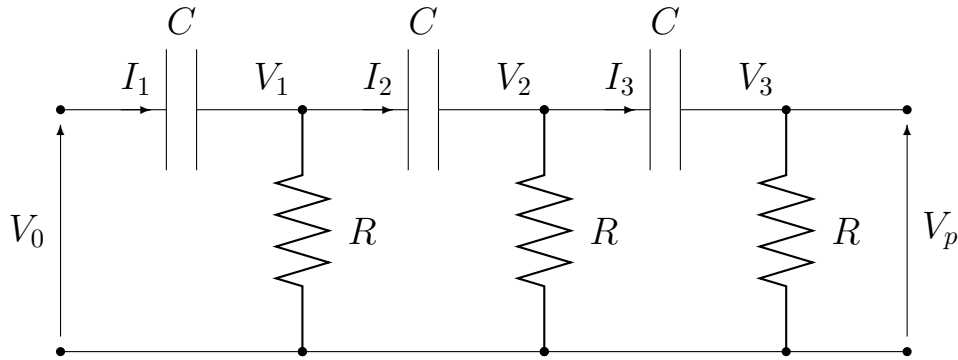- $G(s) = \frac{V_p(s)}{V_0(s)}$  is the transfer function of the following electrical network:



- The electrical network is described by the following differential and static equations:


$$I_1 = C \frac{d(V_0 - V_1)}{dt}, \quad I_2 = C \frac{d(V_1 - V_2)}{dt}, \quad I_3 = C \frac{d(V_2 - V_3)}{dt}$$

$$V_1 = R(I_1 - I_2), \quad V_2 = R(I_2 - I_3), \quad V_3 = RI_3$$

- Using the Laplace transforms, the three differential equations can be expressed as follows:

$$I_1 = C s (V_0 - V_1), \quad I_2 = C s (V_1 - V_2), \quad I_3 = C s (V_2 - V_3)$$

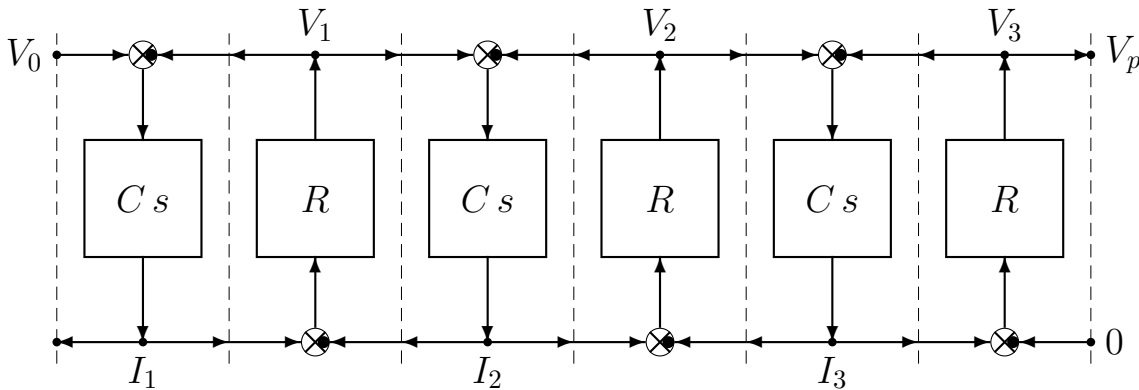- The mathematical model of the considered physical system can be expressed as follows:





- The transfer function  $G(s)$  which links the input  $V_0(s)$  to the output  $V_p(s)$  can be easily obtained using the Mason formula:

$$G(s) = \frac{V_p(s)}{V_0(s)} = \frac{R^3 C^3 s^3}{1 + 5 R C s + 6 R^2 C^2 s^2 + R^3 C^3 s^3}$$

In fact, the block diagram shows 5 rings with gain  $-RCs$ , 6 pairs of rings that do not touch each other, and one set of rings that do not touch three to three. Moreover, the only path starting from  $V_0$  and arriving at  $V_p$  crosses all the blocks.

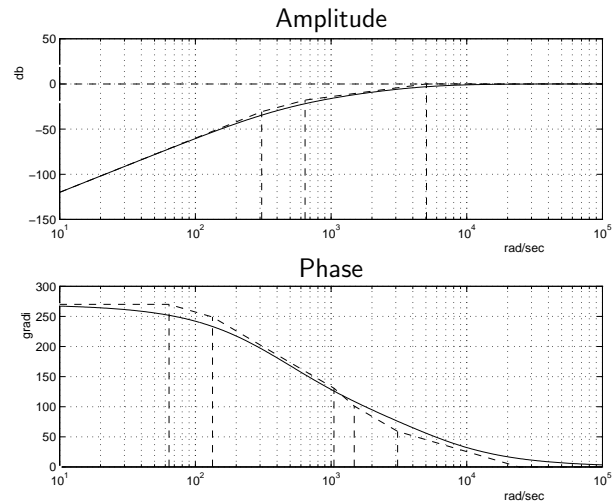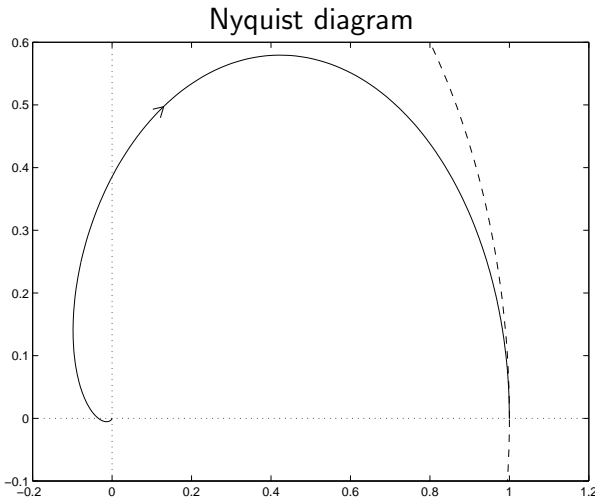- Nyquist Diagram and Bode Diagrams of function  $G(s)$ :



The Bode diagram intersects the real negative axis at point  $\sigma^* = -1/K^*$  characterized by frequency  $\omega^*$ . The values of parameters  $K^*$  and  $\omega^*$  can be easily calculated using the Routh criterion. The characteristic equation  $1 + K G(s) = 0$  of the system is:

$$R^3 C^3 (K + 1) s^3 + 6 R^2 C^2 s^2 + 5 R C s + 1 = 0$$

From the Routh table:

$$\begin{array}{c|cc} 3 & R^3 C^3 (K + 1) & 5 R C \\ 2 & 6 R^2 C^2 & 1 \\ 1 & (30 - 1 - K) R^3 C^3 & \\ 0 & 1 & \end{array}$$

one obtains that the system is stable for  $-1 < K < K^* = 29$ .


- A limit cycle appears in the system if:

$$\boxed{\beta > K^*} \quad \text{dove} \quad \beta = \frac{R_1}{R} \quad \text{e} \quad K^* = 29$$

- The frequency  $\omega^*$  can be obtained solving the following auxiliary equation:

$$6 R^2 C^2 s^2 + 1 = 0 \quad \rightarrow \quad \boxed{\omega^* = \frac{1}{R C \sqrt{6}}}$$

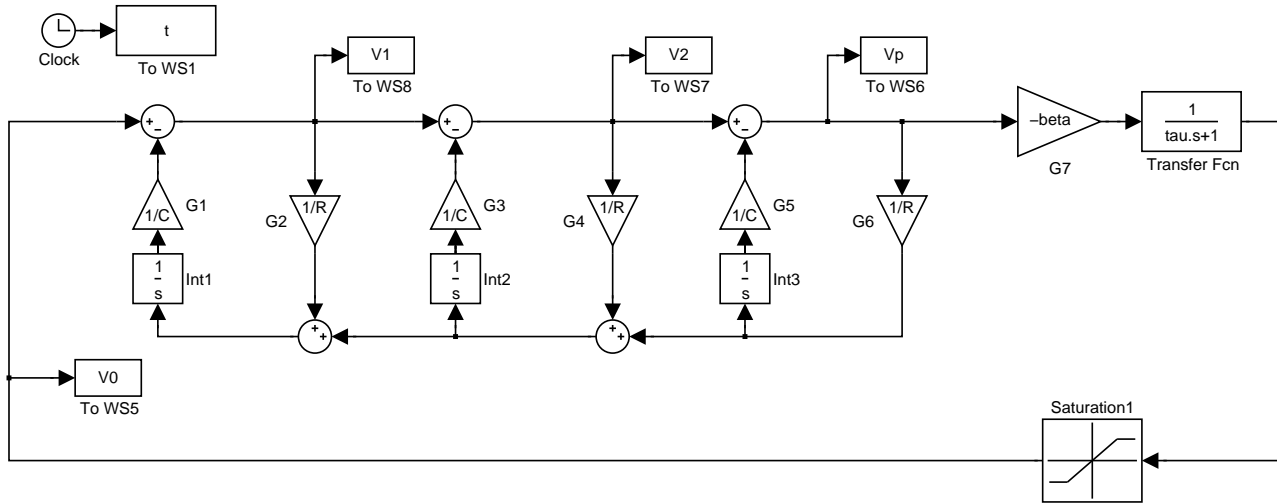- Simulink block scheme of the considered nonlinear system (Phase\_Shift\_Oscillator.mdl):



- Simulation parameters (Phase\_Shift\_Oscillator\_m):

```

R=1; % Resistance
C=0.001; % Capacity
beta=60; % Gain
VM=12; % Maximum voltage
V30=0.1; % Initial condition
Q30=C*V30; % Initial condition
wstar=1/(R*C*sqrt(6)); % Oscillation pulse
tau=0.000001; % Amplifier time constant
Tfin=10*2*pi/wstar; % Duration of the simulation
sim('Phase_Shift_Oscillator_mdl',Tfin) % Simulation
figure(1) % Opening of the figure nr. 1
subplot(211); plot(t,V0); % Plot of voltage V0
subplot(212); plot(t,Vp); % Plot of voltage Vp

```

- Simulation results (variables  $V_n$  and  $V_{\hat{n}}$ ):

Let us choose:

$$R = 1, \quad C = 0.001$$

$$\beta = 60, \quad V_M = 12$$

One obtains:

$$\omega^* = 408.2$$

$$T = 15.4 \text{ ms}$$

