
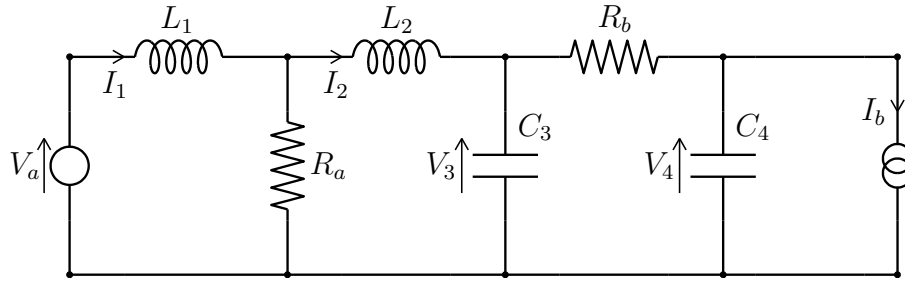


Simple Examples of POG Modeling

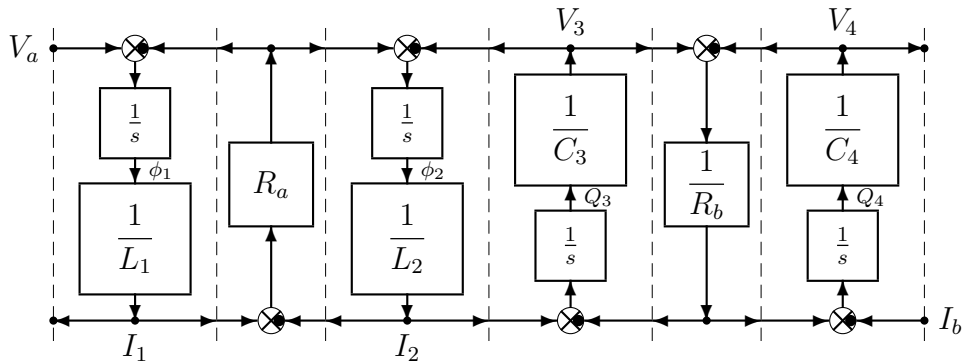- Consider the following electric circuit composed by the inductances L_1, L_2 , the capacities C_3, C_4 , the resistances R_a, R_b , the input voltage V_a and the output current I_b :




The POG model of the given electric circuit is the following:



Let $\mathbf{x} = [I_1 \ I_2 \ V_3 \ V_4]^T$ be the state vector (composed by the output power variables of the dynamic elements) and let $\mathbf{u} = [V_a \ I_b]^T$ be the input vector. Write the corresponding dynamic system $\bar{\mathbf{L}}\dot{\mathbf{x}} = \bar{\mathbf{A}}\mathbf{x} + \bar{\mathbf{B}}\mathbf{u}$ in the state space:


$$\underbrace{\begin{bmatrix} L_1 & 0 & 0 & 0 \\ 0 & L_2 & 0 & 0 \\ 0 & 0 & C_3 & 0 \\ 0 & 0 & 0 & C_4 \end{bmatrix}}_{\bar{\mathbf{L}}} \underbrace{\begin{bmatrix} \dot{I}_1 \\ \dot{I}_2 \\ \dot{V}_3 \\ \dot{V}_4 \end{bmatrix}}_{\dot{\mathbf{x}}} = \underbrace{\begin{bmatrix} -R_a & R_a & 0 & 0 \\ R_a & -R_a & -1 & 0 \\ 0 & 1 & -\frac{1}{R_b} & \frac{1}{R_b} \\ 0 & 0 & \frac{1}{R_b} & -\frac{1}{R_b} \end{bmatrix}}_{\bar{\mathbf{A}}} \underbrace{\begin{bmatrix} I_1 \\ I_2 \\ V_3 \\ V_4 \end{bmatrix}}_{\mathbf{x}} + \underbrace{\begin{bmatrix} 1 & 0 \\ 0 & 0 \\ 0 & 0 \\ 0 & -1 \end{bmatrix}}_{\bar{\mathbf{B}}} \underbrace{\begin{bmatrix} V_a \\ I_b \end{bmatrix}}_{\mathbf{u}}$$

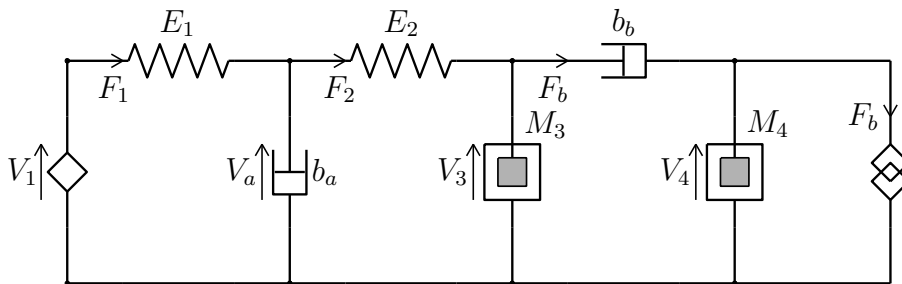- Analogy:** direct correspondence between Electrical and Mechanical physical domains:




The physical domain is different (Mechanical), but the mathematical model is the same if $V_1 = V_a$, $E_1 = L_1$, $E_2 = L_2$, $M_3 = C_3$, $M_4 = C_4$, $F_b = I_b$, $F_1 = I_1$, $F_2 = I_2$, $b_a = R_a$ and $b_b = R_b$.

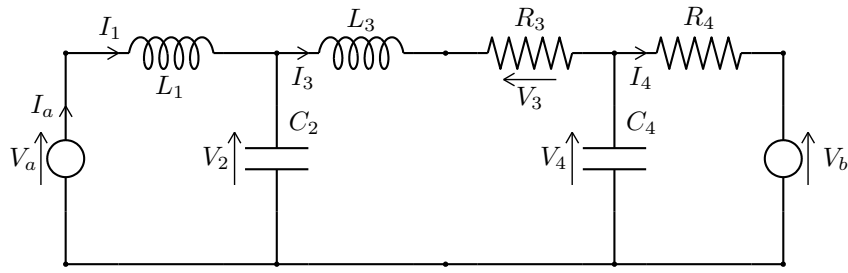2. Consider the following electric circuit composed by the inductances L_1, L_3 , the capacities C_2, C_3 and the resistances R_3 and R_4 . Two inputs act on the system: the voltage V_a and the voltage V_b . The outputs of the system are: the current I_a and the current $I_b = I_4$.



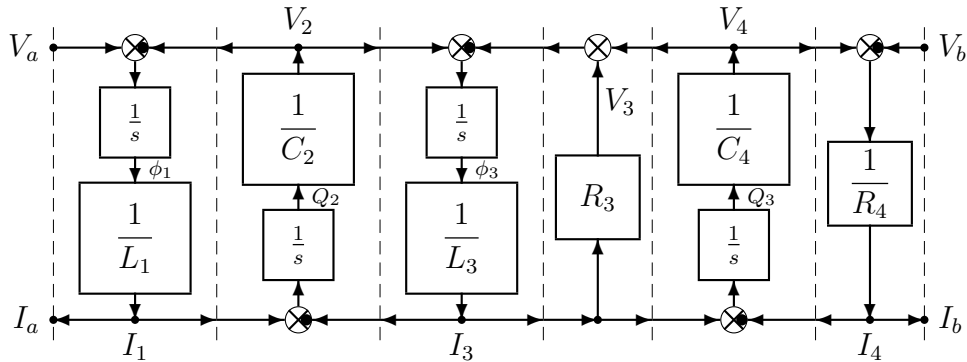The POG model of the given electric circuit is the following:




Let $\mathbf{x} = [I_1 \ V_2 \ I_3 \ V_4]^T$ be the state vector, $\mathbf{u} = [V_a \ V_b]^T$ the input vector and $\mathbf{y} = [I_a \ I_b]^T$ the output vector. Write the corresponding dynamic system $\bar{\mathbf{L}}\dot{\mathbf{x}} = \bar{\mathbf{A}}\mathbf{x} + \bar{\mathbf{B}}\mathbf{u}$ and $\mathbf{y} = \bar{\mathbf{C}}\mathbf{x} + \bar{\mathbf{D}}\mathbf{u}$ in the state space:

$$\underbrace{\begin{bmatrix} L_1 & 0 & 0 & 0 \\ 0 & C_2 & 0 & 0 \\ 0 & 0 & L_3 & 0 \\ 0 & 0 & 0 & C_4 \end{bmatrix}}_{\bar{\mathbf{L}}} \underbrace{\begin{bmatrix} \dot{I}_1 \\ \dot{V}_2 \\ \dot{I}_3 \\ \dot{V}_4 \end{bmatrix}}_{\dot{\mathbf{x}}} = \underbrace{\begin{bmatrix} 0 & -1 & 0 & 0 \\ 1 & 0 & -1 & 0 \\ 0 & 1 & -R_3 & -1 \\ 0 & 0 & 1 & -\frac{1}{R_4} \end{bmatrix}}_{\bar{\mathbf{A}}} \underbrace{\begin{bmatrix} I_1 \\ V_2 \\ I_3 \\ V_4 \end{bmatrix}}_{\mathbf{x}} + \underbrace{\begin{bmatrix} 1 & 0 \\ 0 & 0 \\ 0 & 0 \\ 0 & \frac{1}{R_4} \end{bmatrix}}_{\bar{\mathbf{B}}} \underbrace{\begin{bmatrix} V_a \\ V_b \end{bmatrix}}_{\mathbf{u}}$$


$$\underbrace{\begin{bmatrix} I_a \\ I_b \end{bmatrix}}_{\mathbf{y}} = \underbrace{\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{R_4} \end{bmatrix}}_{\bar{\mathbf{C}}} \mathbf{x} + \underbrace{\begin{bmatrix} 0 & 0 \\ 0 & -\frac{1}{R_4} \end{bmatrix}}_{\bar{\mathbf{D}}} \underbrace{\begin{bmatrix} V_a \\ V_b \end{bmatrix}}_{\mathbf{u}}$$

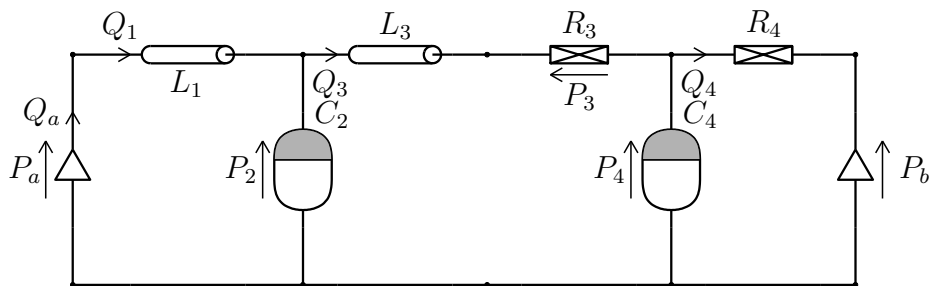- **Analogy:** direct correspondence between Electrical and Hydraulic physical domains:




The physical domain is different (Hydraulic), but the mathematical model is the same if $P_a = V_a, P_b = V_b, P_2 = V_2, P_4 = V_4, Q_a = I_a, Q_1 = I_1, Q_3 = I_3, Q_4 = I_4, .$

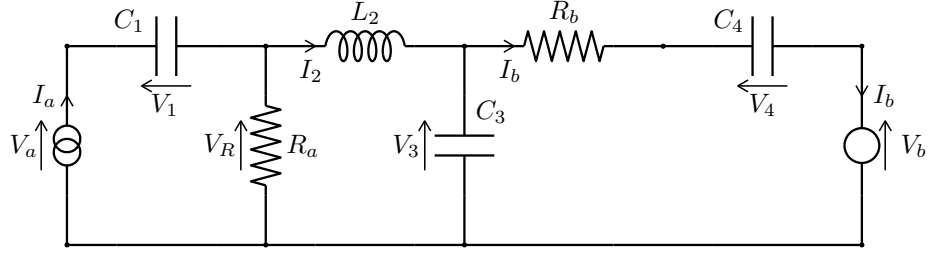3. Consider the following electric circuit composed by the capacities C_1, C_3, C_4 , the inductance L_2 and the resistances R_a and R_b . Two inputs act on the system: the current I_a and the voltage V_b . The outputs of the system are: the voltage V_a and the current I_b .



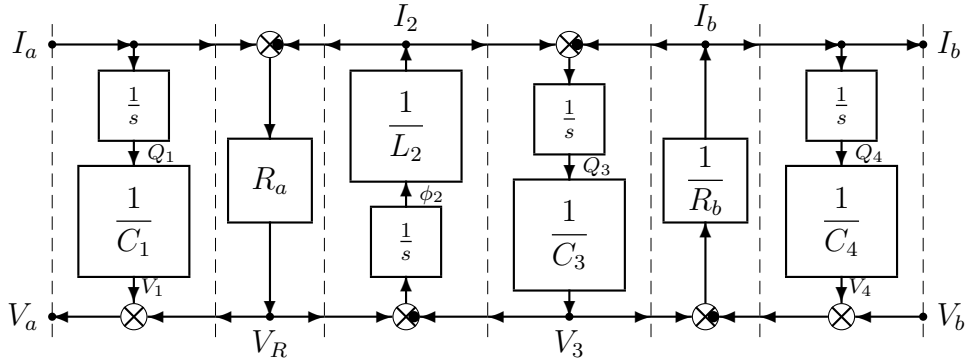The POG model of the given electric circuit is the following:




Let $\mathbf{x} = [V_1 \ I_2 \ V_3 \ V_4]^T$ be the state vector, $\mathbf{u} = [I_a \ V_b]^T$ the input vector and $\mathbf{y} = [V_a \ I_b]^T$ the output vector. Write the corresponding dynamic system $\bar{\mathbf{L}}\dot{\mathbf{x}} = \bar{\mathbf{A}}\mathbf{x} + \bar{\mathbf{B}}\mathbf{u}$ and $\mathbf{y} = \bar{\mathbf{C}}\mathbf{x} + \bar{\mathbf{D}}\mathbf{u}$ in the state space:


$$\underbrace{\begin{bmatrix} C_1 & 0 & 0 & 0 \\ 0 & L_2 & 0 & 0 \\ 0 & 0 & C_3 & 0 \\ 0 & 0 & 0 & C_4 \end{bmatrix}}_{\bar{\mathbf{L}}} \underbrace{\begin{bmatrix} \dot{V}_1 \\ \dot{I}_2 \\ \dot{V}_3 \\ \dot{V}_4 \end{bmatrix}}_{\dot{\mathbf{x}}} = \underbrace{\begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & -R_a & -1 & 0 \\ 0 & 1 & -\frac{1}{R_b} & \frac{1}{R_b} \\ 0 & 0 & \frac{1}{R_b} & -\frac{1}{R_b} \end{bmatrix}}_{\bar{\mathbf{A}}} \underbrace{\begin{bmatrix} V_1 \\ I_2 \\ V_3 \\ V_4 \end{bmatrix}}_{\mathbf{x}} + \underbrace{\begin{bmatrix} 1 & 0 \\ R_a & 0 \\ 0 & \frac{1}{R_b} \\ 0 & -\frac{1}{R_b} \end{bmatrix}}_{\bar{\mathbf{B}}} \underbrace{\begin{bmatrix} I_a \\ V_b \end{bmatrix}}_{\mathbf{u}}$$

$$\underbrace{\begin{bmatrix} V_a \\ I_b \end{bmatrix}}_{\mathbf{y}} = \underbrace{\begin{bmatrix} 1 & -R_a & 0 & 0 \\ 0 & 0 & \frac{1}{R_b} & -\frac{1}{R_b} \end{bmatrix}}_{\bar{\mathbf{C}}} \mathbf{x} + \underbrace{\begin{bmatrix} R_a & 0 \\ 0 & -\frac{1}{R_b} \end{bmatrix}}_{\bar{\mathbf{D}}} \underbrace{\begin{bmatrix} I_a \\ V_b \end{bmatrix}}_{\mathbf{u}}$$

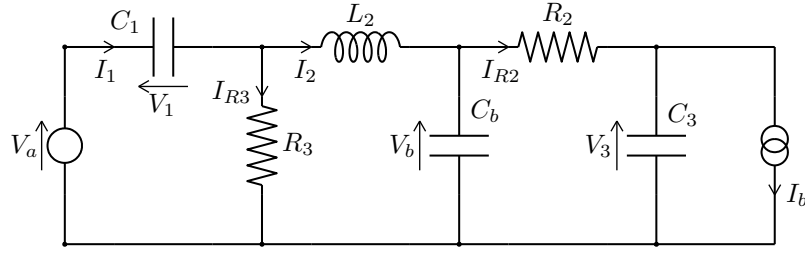4. Consider the following electric circuit composed by the capacities C_1, C_b, C_3 and the resistances R_2 and R_3 . Two inputs act on the system: the voltage V_a and the current I_b . The outputs of the system are: the current I_1 and the voltage V_3 .



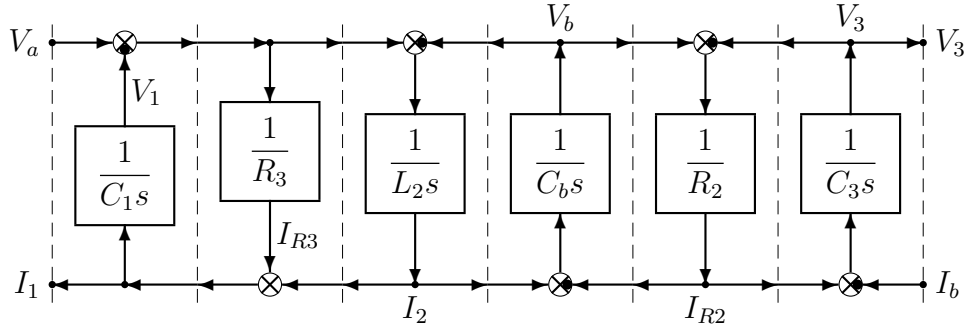The POG model of the given electric circuit is the following:




Let $\mathbf{x} = [V_1 \ I_2 \ V_b \ V_3]^T$ be the state vector, $\mathbf{u} = [V_a \ I_b]^T$ the input vector and $\mathbf{y} = [I_1 \ V_3]^T$ the output vector. Write the corresponding dynamic system $\bar{\mathbf{L}}\dot{\mathbf{x}} = \bar{\mathbf{A}}\mathbf{x} + \bar{\mathbf{B}}\mathbf{u}$ and $\mathbf{y} = \bar{\mathbf{C}}\mathbf{x} + \bar{\mathbf{D}}\mathbf{u}$ in the state space:


$$\underbrace{\begin{bmatrix} C_1 & 0 & 0 & 0 \\ 0 & L_2 & 0 & 0 \\ 0 & 0 & C_b & 0 \\ 0 & 0 & 0 & C_3 \end{bmatrix}}_{\bar{\mathbf{L}}} \underbrace{\begin{bmatrix} \dot{V}_1 \\ \dot{I}_2 \\ \dot{V}_b \\ \dot{V}_3 \end{bmatrix}}_{\dot{\mathbf{x}}} = \underbrace{\begin{bmatrix} -\frac{1}{R_3} & 1 & 0 & 0 \\ -1 & 0 & -1 & 0 \\ 0 & 1 & -\frac{1}{R_2} & \frac{1}{R_2} \\ 0 & 0 & \frac{1}{R_2} & -\frac{1}{R_2} \end{bmatrix}}_{\bar{\mathbf{A}}} \underbrace{\begin{bmatrix} V_1 \\ I_2 \\ V_b \\ V_3 \end{bmatrix}}_{\mathbf{x}} + \underbrace{\begin{bmatrix} \frac{1}{R_3} & 0 \\ 1 & 0 \\ 0 & 0 \\ 0 & -1 \end{bmatrix}}_{\bar{\mathbf{B}}} \underbrace{\begin{bmatrix} V_a \\ I_b \end{bmatrix}}_{\mathbf{u}}$$

$$\underbrace{\begin{bmatrix} I_1 \\ V_3 \end{bmatrix}}_{\mathbf{y}} = \underbrace{\begin{bmatrix} -\frac{1}{R_3} & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 \end{bmatrix}}_{\bar{\mathbf{C}}} \mathbf{x} + \underbrace{\begin{bmatrix} \frac{1}{R_3} & 0 \\ 0 & 0 \end{bmatrix}}_{\bar{\mathbf{D}}} \underbrace{\begin{bmatrix} V_a \\ I_b \end{bmatrix}}_{\mathbf{u}}$$

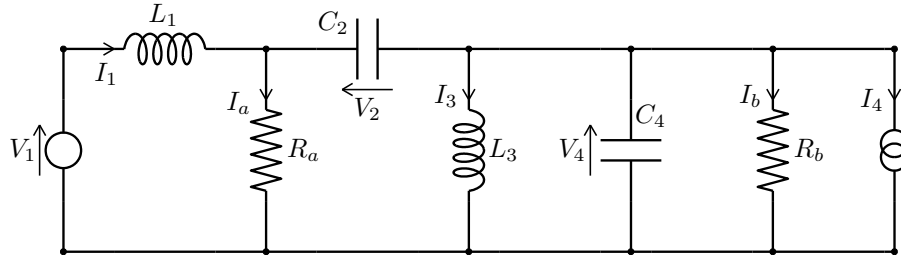5. Consider the following electric circuit composed by the inductances L_1 , L_3 , the capacities C_2 , C_4 and the resistances R_a and R_b . Two inputs act on the system: the voltage V_1 and the current I_4 . The outputs of the system are: the current I_1 and the voltage V_4 .



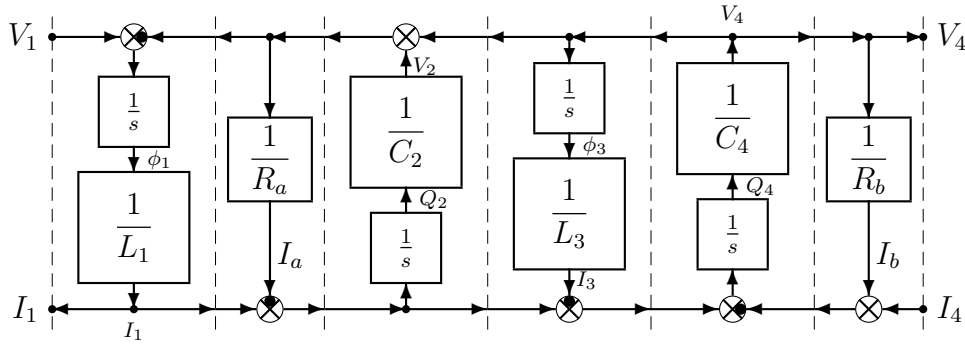The POG model of the given electric circuit has the following structure:




Let $\mathbf{x} = [I_1 \ V_2 \ I_3 \ V_4]^T$ be the state vector, $\mathbf{u} = [V_1 \ I_4]^T$ the input vector and $\mathbf{y} = [I_1 \ V_4]^T$ the output vector. Write the corresponding dynamic system $\bar{\mathbf{L}}\dot{\mathbf{x}} = \bar{\mathbf{A}}\mathbf{x} + \bar{\mathbf{B}}\mathbf{u}$ and $\mathbf{y} = \bar{\mathbf{C}}\mathbf{x} + \bar{\mathbf{D}}\mathbf{u}$ in the state space:


$$\underbrace{\begin{bmatrix} L_1 & 0 & 0 & 0 \\ 0 & C_2 & 0 & 0 \\ 0 & 0 & L_3 & 0 \\ 0 & 0 & 0 & C_4 \end{bmatrix}}_{\bar{\mathbf{L}}} \underbrace{\begin{bmatrix} \dot{I}_1 \\ \dot{V}_2 \\ \dot{I}_3 \\ \dot{V}_4 \end{bmatrix}}_{\dot{\mathbf{x}}} = \underbrace{\begin{bmatrix} 0 & -1 & 0 & -1 \\ 1 & -\frac{1}{R_a} & 0 & -\frac{1}{R_a} \\ 0 & 0 & 0 & 1 \\ 1 & -\frac{1}{R_a} & -1 & -\frac{1}{R_a} - \frac{1}{R_b} \end{bmatrix}}_{\bar{\mathbf{A}}} \underbrace{\begin{bmatrix} I_1 \\ V_2 \\ I_3 \\ V_4 \end{bmatrix}}_{\mathbf{x}} + \underbrace{\begin{bmatrix} 1 & 0 \\ 0 & 0 \\ 0 & 0 \\ 0 & -1 \end{bmatrix}}_{\bar{\mathbf{B}}} \underbrace{\begin{bmatrix} V_1 \\ I_4 \end{bmatrix}}_{\mathbf{u}}$$

$$\underbrace{\begin{bmatrix} I_1 \\ V_4 \end{bmatrix}}_{\mathbf{y}} = \underbrace{\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}}_{\bar{\mathbf{C}}} \mathbf{x} + \underbrace{\begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}}_{\bar{\mathbf{D}}} \underbrace{\begin{bmatrix} V_1 \\ I_4 \end{bmatrix}}_{\mathbf{u}}$$

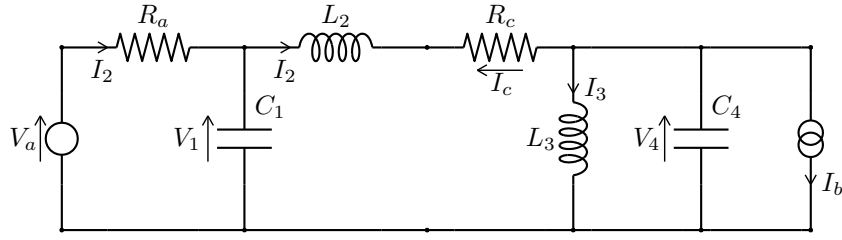6. Consider the following electric circuit composed by the capacities C_1, C_4 , the inductances L_2, L_3 and the resistances R_a, R_b and R_c . Two inputs act on the system: the voltage V_a and the current I_b . The outputs of the system are: the current I_a and the voltage V_b .



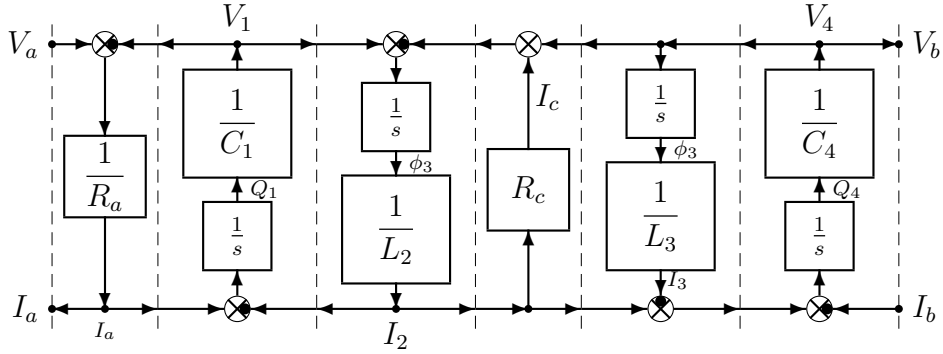The POG model of the given electric circuit has the following structure:




Let $\mathbf{x} = [V_1 \ I_2 \ I_3 \ V_4]^T$ be the state vector, $\mathbf{u} = [V_a \ I_b]^T$ the input vector and $\mathbf{y} = [I_a \ V_b]^T$ the output vector. Write the corresponding dynamic system $\bar{\mathbf{L}}\dot{\mathbf{x}} = \bar{\mathbf{A}}\mathbf{x} + \bar{\mathbf{B}}\mathbf{u}$ and $\mathbf{y} = \bar{\mathbf{C}}\mathbf{x} + \bar{\mathbf{D}}\mathbf{u}$ in the state space:


$$\underbrace{\begin{bmatrix} C_1 & 0 & 0 & 0 \\ 0 & L_2 & 0 & 0 \\ 0 & 0 & L_3 & 0 \\ 0 & 0 & 0 & C_4 \end{bmatrix}}_{\bar{\mathbf{L}}} \underbrace{\begin{bmatrix} \dot{V}_1 \\ \dot{I}_2 \\ \dot{I}_3 \\ \dot{V}_4 \end{bmatrix}}_{\dot{\mathbf{x}}} = \underbrace{\begin{bmatrix} -\frac{1}{R_a} & -1 & 0 & 0 \\ 1 & -R_c & 0 & -1 \\ 0 & 0 & 0 & 1 \\ 0 & 1 & -1 & 0 \end{bmatrix}}_{\bar{\mathbf{A}}} \underbrace{\begin{bmatrix} V_1 \\ I_2 \\ I_3 \\ V_4 \end{bmatrix}}_{\mathbf{x}} + \underbrace{\begin{bmatrix} \frac{1}{R_a} & 0 \\ 0 & 0 \\ 0 & 0 \\ 0 & -1 \end{bmatrix}}_{\bar{\mathbf{B}}} \underbrace{\begin{bmatrix} V_a \\ I_b \end{bmatrix}}_{\mathbf{u}}$$

$$\underbrace{\begin{bmatrix} I_a \\ V_b \end{bmatrix}}_{\mathbf{y}} = \underbrace{\begin{bmatrix} -\frac{1}{R_a} & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 \end{bmatrix}}_{\bar{\mathbf{C}}} \mathbf{x} + \underbrace{\begin{bmatrix} \frac{1}{R_a} & 0 \\ 0 & 0 \end{bmatrix}}_{\bar{\mathbf{D}}} \underbrace{\begin{bmatrix} V_a \\ I_b \end{bmatrix}}_{\mathbf{u}}$$

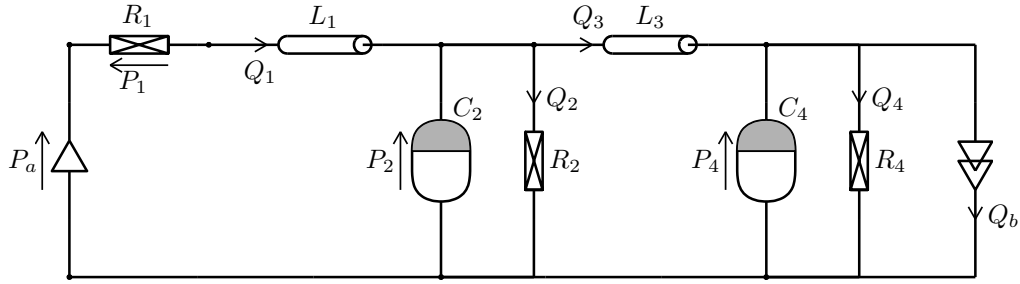7. Consider the following hydraulic circuit composed by the hydraulic inductances L_1, L_3 , the hydraulic capacities C_2, C_4 and the hydraulic resistances R_1, R_2, R_4, R_5 and R_6 . Two inputs act on the system: the pressure P_a and the volume flow rate Q_b . The outputs of the system are: the volume flow rate $Q_a = Q_1 + Q_5$ and the pressure $P_b = P_4$.



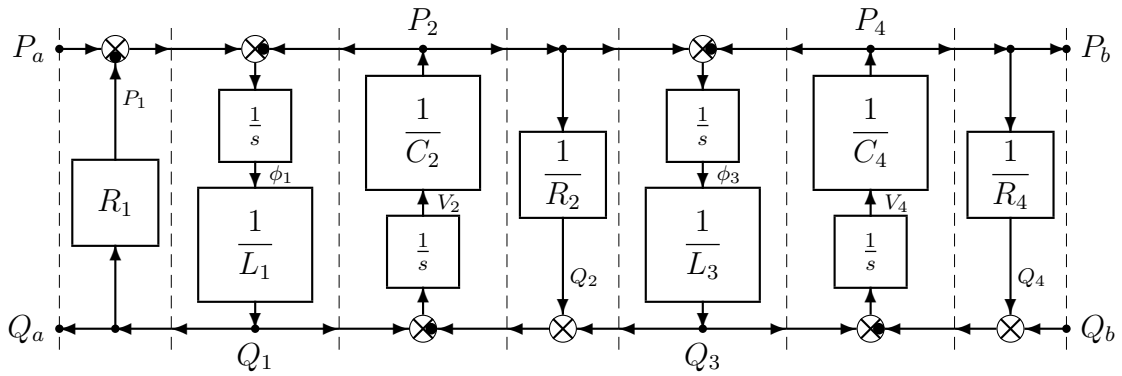The POG model of the given hydraulic circuit has the following structure:




Let $\mathbf{x} = [Q_1 \ P_2 \ Q_3 \ P_4]^T$ be the state vector, $\mathbf{u} = [P_a \ Q_b]^T$ the input vector and $\mathbf{y} = [Q_a \ P_b]^T$ the output vector. Write the corresponding dynamic system $\bar{\mathbf{L}}\dot{\mathbf{x}} = \bar{\mathbf{A}}\mathbf{x} + \bar{\mathbf{B}}\mathbf{u}$ and $\mathbf{y} = \bar{\mathbf{C}}\mathbf{x} + \bar{\mathbf{D}}\mathbf{u}$ in the state space:


$$\underbrace{\begin{bmatrix} L_1 & 0 & 0 & 0 \\ 0 & C_2 & 0 & 0 \\ 0 & 0 & L_3 & 0 \\ 0 & 0 & 0 & C_4 \end{bmatrix}}_{\bar{\mathbf{L}}} \underbrace{\begin{bmatrix} \dot{Q}_1 \\ \dot{P}_2 \\ \dot{Q}_3 \\ \dot{P}_4 \end{bmatrix}}_{\dot{\mathbf{x}}} = \underbrace{\begin{bmatrix} -R_1 & -1 & 0 & 0 \\ 1 & -\frac{1}{R_2} & -1 & 0 \\ 0 & 1 & 0 & -1 \\ 0 & 0 & 1 & -\frac{1}{R_4} \end{bmatrix}}_{\bar{\mathbf{A}}} \underbrace{\begin{bmatrix} Q_1 \\ P_2 \\ Q_3 \\ P_4 \end{bmatrix}}_{\mathbf{x}} + \underbrace{\begin{bmatrix} 1 & 0 \\ 0 & 0 \\ 0 & 0 \\ 0 & -1 \end{bmatrix}}_{\bar{\mathbf{B}}} \underbrace{\begin{bmatrix} P_a \\ Q_b \end{bmatrix}}_{\mathbf{u}}$$

$$\underbrace{\begin{bmatrix} Q_a \\ P_b \end{bmatrix}}_{\mathbf{y}} = \underbrace{\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}}_{\bar{\mathbf{C}}} \mathbf{x} + \underbrace{\begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}}_{\bar{\mathbf{D}}} \underbrace{\begin{bmatrix} P_a \\ Q_b \end{bmatrix}}_{\mathbf{u}}$$

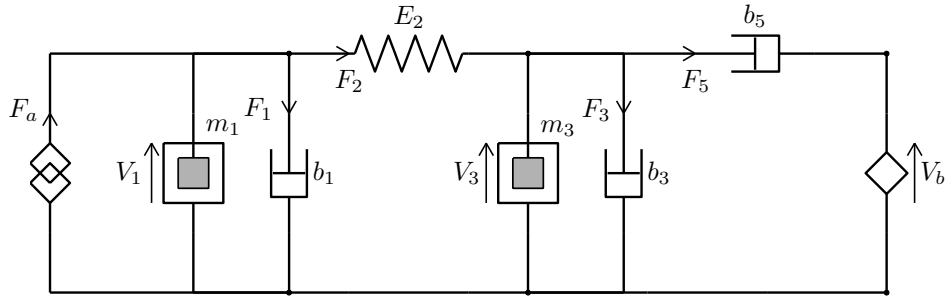8. Consider the following mechanical system composed by masses m_1 , m_3 , elasticity E_4 and dampers b_1 , b_2 and b_5 . Two inputs act on the system: the force F_a and the velocity V_b . The outputs of the system are: velocity V_1 and the force F_5 .



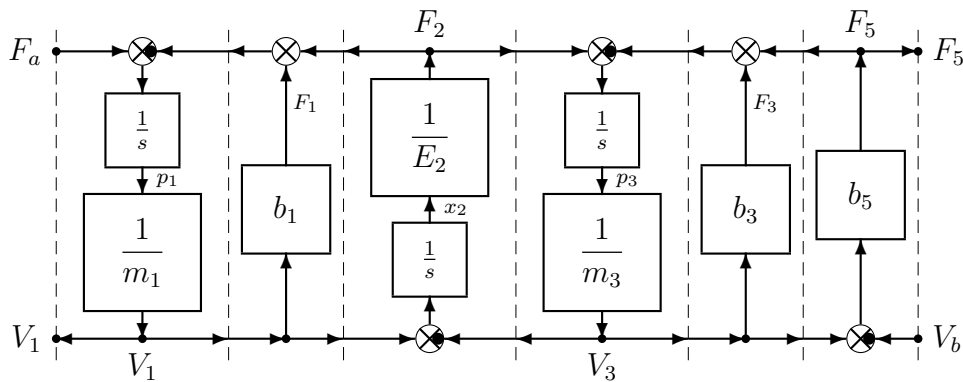The POG model of the given mechanical system has the following structure:




Let $\mathbf{x} = [V_1 \ F_2 \ V_3]^T$ be the state vector, $\mathbf{u} = [F_a \ V_b]^T$ the input vector and $\mathbf{y} = [V_1 \ F_5]^T$ the output vector. Write the corresponding dynamic system $\bar{\mathbf{L}}\dot{\mathbf{x}} = \bar{\mathbf{A}}\mathbf{x} + \bar{\mathbf{B}}\mathbf{u}$ and $\mathbf{y} = \bar{\mathbf{C}}\mathbf{x} + \bar{\mathbf{D}}\mathbf{u}$ in the state space:


$$\underbrace{\begin{bmatrix} m_1 & 0 & 0 \\ 0 & E_2 & 0 \\ 0 & 0 & m_3 \end{bmatrix}}_{\bar{\mathbf{L}}} \underbrace{\begin{bmatrix} \dot{V}_1 \\ \dot{F}_2 \\ \dot{V}_3 \end{bmatrix}}_{\dot{\mathbf{x}}} = \underbrace{\begin{bmatrix} -b_1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & 1 & -b_3 - b_5 \end{bmatrix}}_{\bar{\mathbf{A}}} \underbrace{\begin{bmatrix} V_1 \\ F_2 \\ V_3 \end{bmatrix}}_{\mathbf{x}} + \underbrace{\begin{bmatrix} 1 & 0 \\ 0 & 0 \\ 0 & b_5 \end{bmatrix}}_{\bar{\mathbf{B}}} \underbrace{\begin{bmatrix} F_a \\ V_b \end{bmatrix}}_{\mathbf{u}}$$

$$\underbrace{\begin{bmatrix} V_1 \\ F_5 \end{bmatrix}}_{\mathbf{y}} = \underbrace{\begin{bmatrix} 1 & 0 & 0 \\ 0 & 0 & b_5 \end{bmatrix}}_{\bar{\mathbf{C}}} \mathbf{x} + \underbrace{\begin{bmatrix} 1 & 0 \\ 0 & -b_5 \end{bmatrix}}_{\bar{\mathbf{D}}} \underbrace{\begin{bmatrix} F_a \\ V_b \end{bmatrix}}_{\mathbf{u}}$$

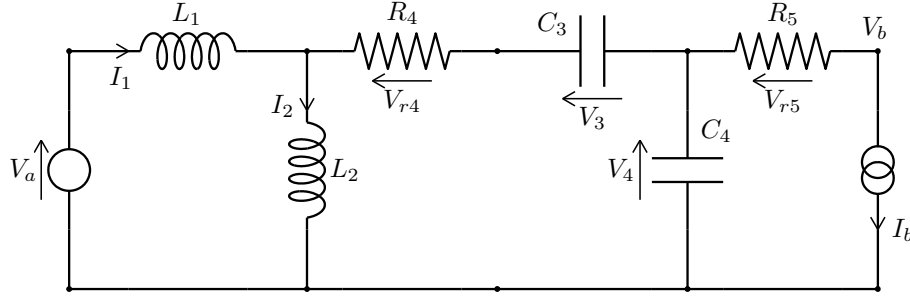9. Consider the following electric circuit composed by the inductances L_1, L_2 , the capacities C_3, C_4 and the resistances R_1, R_4 and R_5 . Two inputs act on the system: the voltage V_a and the current I_b . The outputs of the system are: the current I_1 and the voltage V_b .



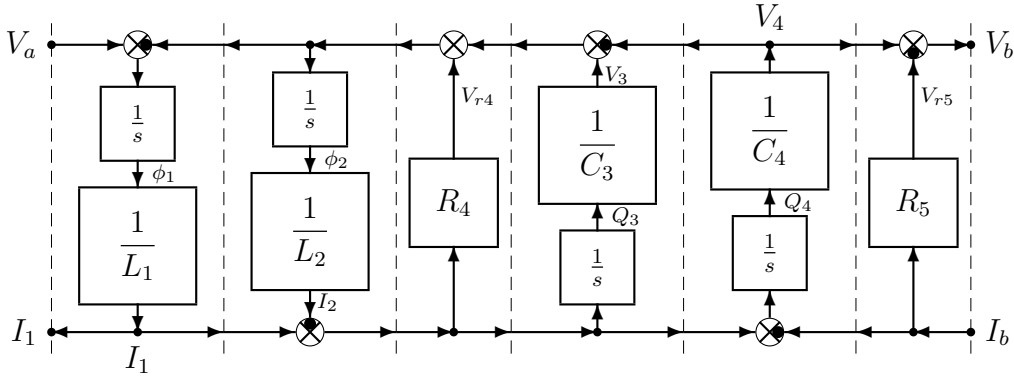The POG model of the given electric circuit has the following structure:



Let $\mathbf{x} = [I_1 \ I_2 \ V_3 \ V_4]^T$ be the state vector, $\mathbf{u} = [V_a \ I_b]^T$ the input vector and $\mathbf{y} = [I_1 \ V_b]^T$ the output vector. Write the corresponding dynamic system $\bar{\mathbf{L}}\dot{\mathbf{x}} = \bar{\mathbf{A}}\mathbf{x} + \bar{\mathbf{B}}\mathbf{u}$ and $\mathbf{y} = \bar{\mathbf{C}}\mathbf{x} + \bar{\mathbf{D}}\mathbf{u}$ in the state space:

$$\underbrace{\begin{bmatrix} L_1 & 0 & 0 & 0 \\ 0 & L_2 & 0 & 0 \\ 0 & 0 & C_3 & 0 \\ 0 & 0 & 0 & C_4 \end{bmatrix}}_{\bar{\mathbf{L}}} \underbrace{\begin{bmatrix} \dot{I}_1 \\ \dot{I}_2 \\ \dot{V}_3 \\ \dot{V}_4 \end{bmatrix}}_{\dot{\mathbf{x}}} = \underbrace{\begin{bmatrix} -R_4 & R_4 & -1 & -1 \\ R_4 & -R_4 & 1 & 1 \\ 1 & -1 & 0 & 0 \\ 1 & -1 & 0 & 0 \end{bmatrix}}_{\bar{\mathbf{A}}} \underbrace{\begin{bmatrix} I_1 \\ I_2 \\ V_3 \\ V_4 \end{bmatrix}}_{\mathbf{x}} + \underbrace{\begin{bmatrix} 1 & 0 \\ 0 & 0 \\ 0 & 0 \\ 0 & -1 \end{bmatrix}}_{\bar{\mathbf{B}}} \underbrace{\begin{bmatrix} V_a \\ I_b \end{bmatrix}}_{\mathbf{u}}$$

$$\underbrace{\begin{bmatrix} I_1 \\ V_b \end{bmatrix}}_{\mathbf{y}} = \underbrace{\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}}_{\bar{\mathbf{C}}} \mathbf{x} + \underbrace{\begin{bmatrix} 0 & 0 \\ 0 & -R_5 \end{bmatrix}}_{\bar{\mathbf{D}}} \underbrace{\begin{bmatrix} V_a \\ I_b \end{bmatrix}}_{\mathbf{u}}$$